

Series Resistors

Applied Mechatronics

First Grade Level

Wolfgang Neff

Series Resistors (1)

- Current Limiting Resistors
 - Devices can break if current is too high
 - Series resistors limit the current
 - They protect the device from damage
- Example LED
 - Supply voltage $V_S = 5\text{ V}$
 - From datasheet for LED L-63ID
 - Typical forward voltage $V_F = 1.9\text{ V}$
 - Typical forward current $I_F = 10\text{ mA}$
 - Maximum forward current $I_F = 30\text{ mA}$

Series Resistors (2)

- Derivation of the formula of the Series Resistor

- Given values

- I_F , V_F , V_S

- Required values


- R_S

- Relations

- $I_R = I_F$
- $V_S = V_R + V_F$
- $R_S = V_R / I_R$

- Formula

- $$R_S = \frac{V_S - V_F}{I_F}$$

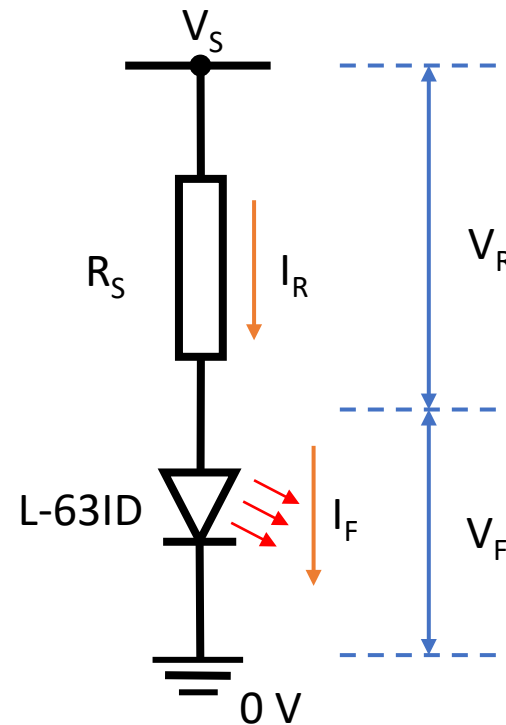

Series Resistors (3)

- Calculation of the Series Resistor


- Given values

- $V_S = 5\text{ V}$
- $V_F = 1.9\text{ V}$
- $I_F = 10\text{ mA}$

- Solution


- $R_S = \frac{V_S - V_F}{I_F}$
- $R_S = \frac{5\text{ V} - 1.9\text{ V}}{10\text{ mA}} = \frac{3.1\text{ V}}{0.01\text{ A}}$
- $R_S = 310\ \Omega \rightarrow 330\ \Omega$

E12 Series of Resistors

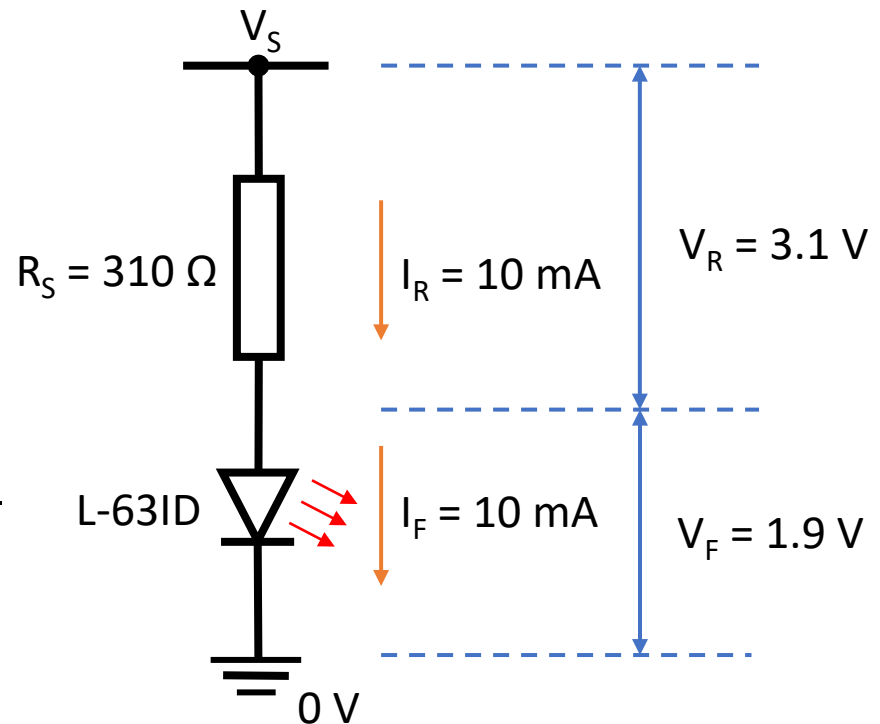

Series Resistors (4)

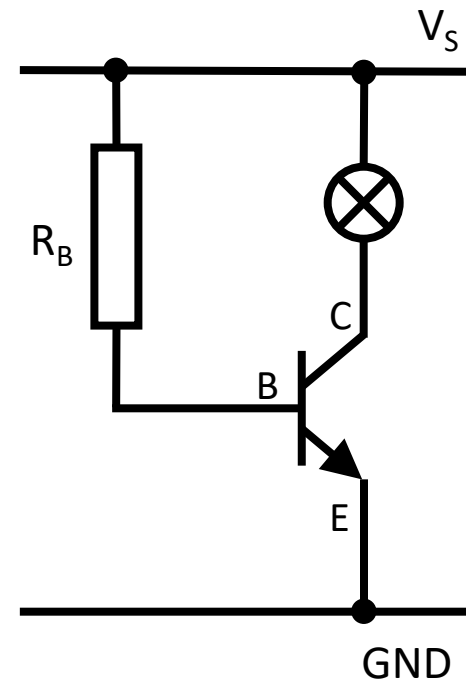- Example Base Resistor
 - Supply voltage $V_S = 5\text{ V}$
 - Load current $I_L = 350\text{ mA}$
 - From datasheet for BC377-40
 - DC Current Gain $h_{FE} = 250$
 - Saturation Voltage $V_{BE} = 0.7\text{ V}$



Series Resistors (5)

- Derivation of the formula of the Series Resistor

- Given values

- h_{FE}, I_C, V_{BE}, V_S

- Required values


- I_B, R_B

- Relations

- $I_C = h_{FE} \cdot I_B$
- $V_S = V_B + V_{BE}$
- $R_B = V_B / I_B$

- Formula

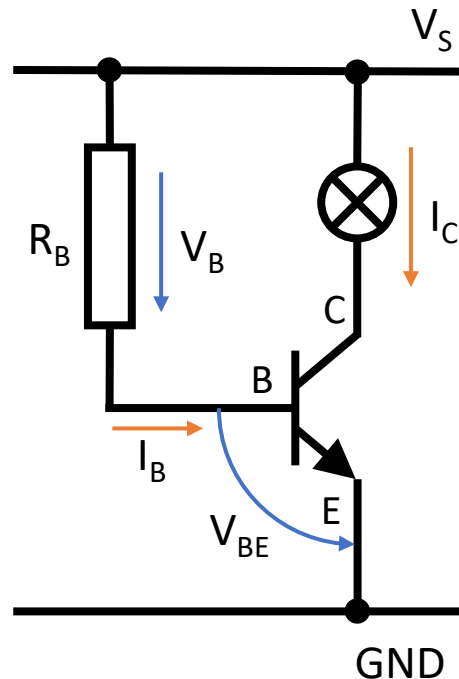- $$R_B = \frac{V_S - V_{BE}}{I_C / h_{FE}} = h_{FE} \cdot \frac{V_S - V_{BE}}{I_C} = \frac{V_S - V_{BE}}{I_B}$$



I_C : Collector Current = Load Current

I_B : Base Current

R_B : Base Resistor

V_B : Base Resistor Voltage

Series Resistors (6)


- Calculation of the Series Resistor

- Given values

- $V_S = 5\text{ V}$
 - $I_C = 350\text{ mA}$
 - $h_{FE} = 250$
 - $V_{BE} = 0.7\text{ V}$

- Solution

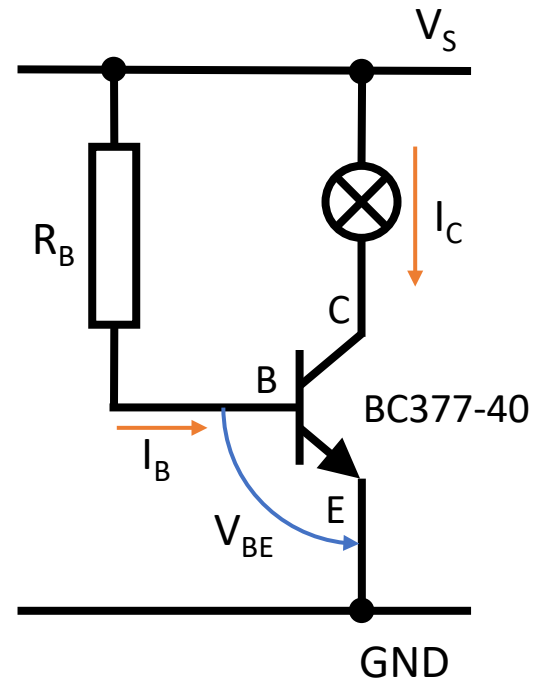- $I_B = \frac{I_C}{h_{FE}} = 1.4\text{ mA}$
 - $R_B = \frac{V_S - V_{BE}}{I_B}$
 $= 3071\ \Omega \rightarrow 2.7\text{ k}\Omega$



E12 Series