

# Capacitors and Inductors


Electrical Engineering

Third Grade Level

Wolfgang Neff
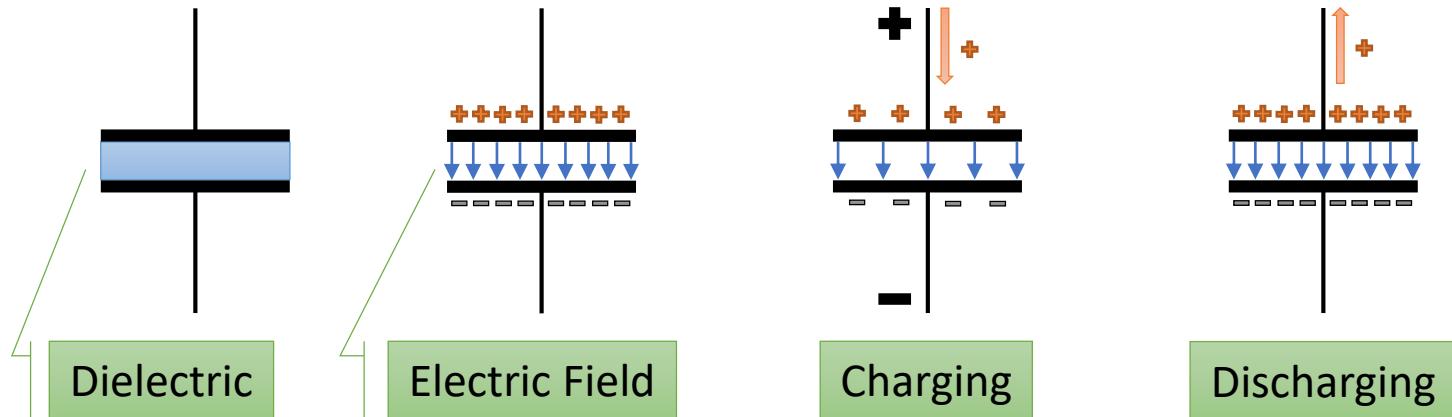
# Capacitors (1)

- Basic Features
  - Accumulates electric charges on two surfaces
    - The surfaces are insulated from each other
  - Stores electrical energy in an electric field
  - It can be charged and discharged



# Capacitors (2)

- Charging
  - Basic Relations

$$\bullet R = \frac{U}{I}$$

$$\bullet I = \frac{dQ}{dt} = \dot{Q}$$

$$\bullet Q = C \cdot U$$


- Kirchhoff's circuit law

$$\bullet U_R + U_C - U = 0$$

$$\bullet R\dot{Q} + \frac{Q}{C} - U = 0$$



- Differential Equation
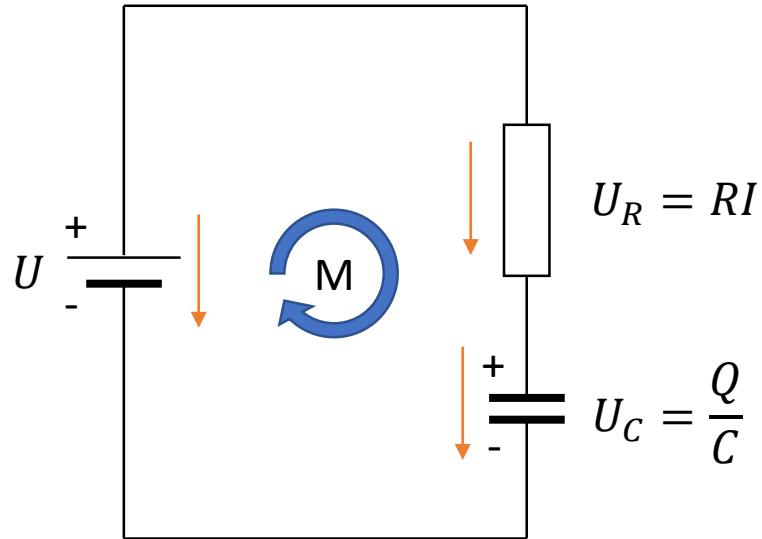
$$\bullet \dot{Q} = \frac{1}{R}U - \frac{1}{RC}Q$$



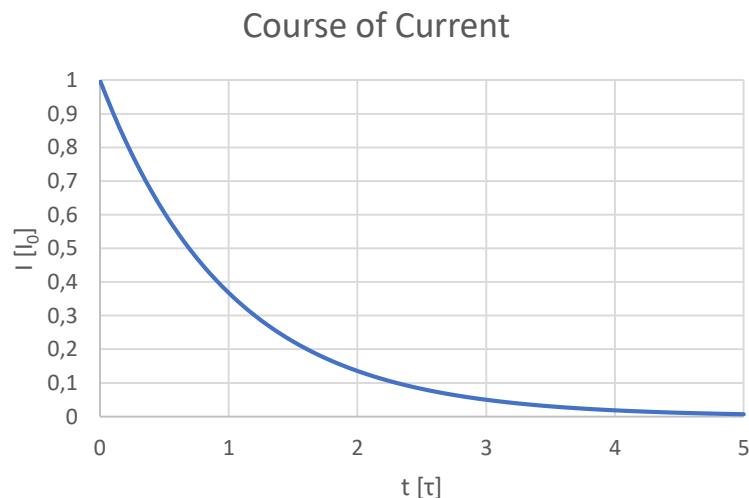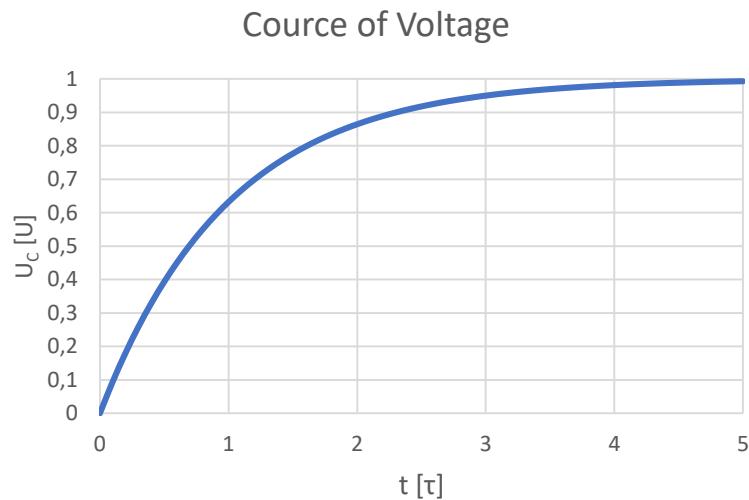
# Capacitors (3)

- Charging (continued)
  - Solution of the equation
    - $Q = CU - CUe^{-\frac{1}{RC}t}$
    - $\tau = RC$  (time constant)
  - Course of the voltage
    - $U_C = \frac{Q}{C}$
    - $U_C = U(1 - e^{-\frac{t}{\tau}})$
  - Course of the current
    - $I = \dot{Q}$
    - $I = \frac{U}{R} e^{-\frac{t}{\tau}}$




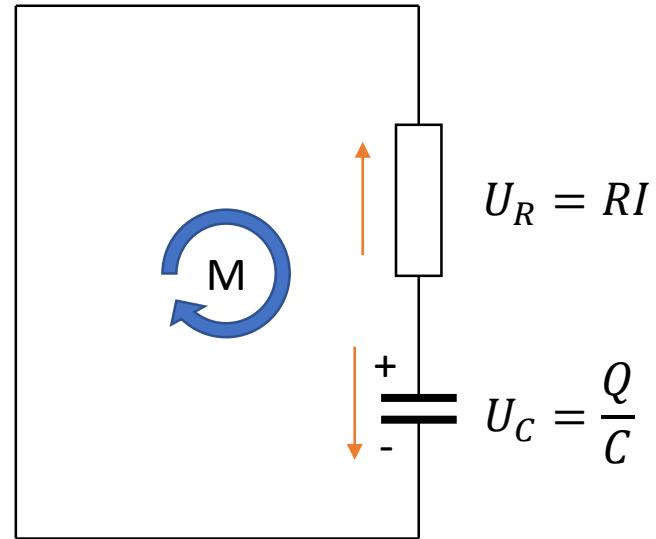
# Capacitors (4)

- Discharging
  - Basic Relations
    - $R = \frac{U}{I}$
    - $I = \frac{dQ}{dt} = \dot{Q}$
    - $Q = C \cdot U$
  - Kirchhoff's circuit law
    - $-U_R + U_C = 0$
    - $-R\dot{Q} + \frac{Q}{C} = 0$
  - Differential Equation
    - $\dot{Q} = -\frac{1}{RC}Q$


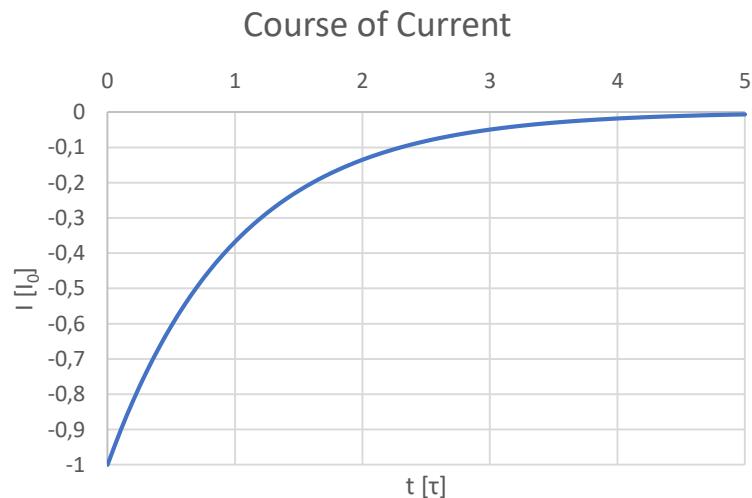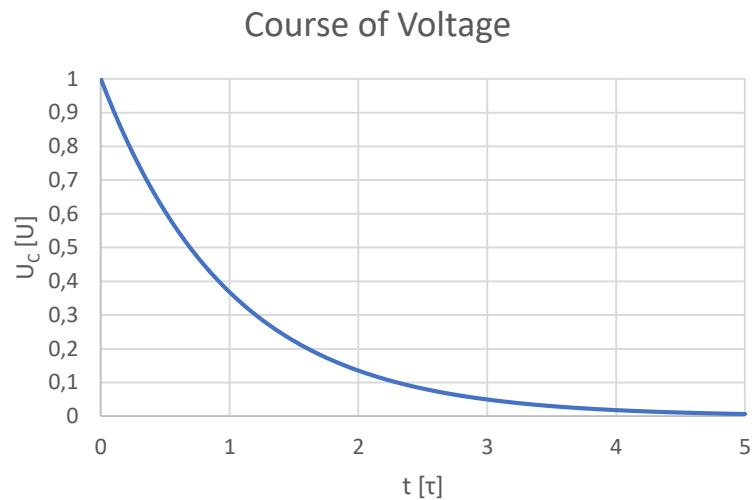
# Capacitors (5)

- Discharging (continued)
  - Solution of the equation
    - $Q = CUe^{-\frac{1}{RC}t}$
    - $\tau = RC$  (time constant)
  - Course of the voltage
    - $U_C = \frac{Q}{C}$
    - $U_C = U(e^{-\frac{t}{\tau}})$
  - Course of the current
    - $I = \dot{Q}$
    - $I = -\frac{U}{R}e^{-\frac{t}{\tau}}$



# Capacitors (6)

- Time Constant

- $\tau = RC$

- Half-value Time

- $e^{-\frac{t_h}{\tau}} = \frac{1}{2}$

- $t_h = \tau \ln 2$

- $t_h = 0.69\tau$

- Full Charge Time

- $t_f = 5\tau$

- $e^{-5} = 0.0067$


- $1 - e^{-5} = 0.993$

| $\tau$    | 0    | 1   | 2   | 3   | 4   | 5   |
|-----------|------|-----|-----|-----|-----|-----|
| Charge    | 0%   | 63% | 86% | 95% | 98% | 99% |
| Discharge | 100% | 37% | 14% | 5%  | 2%  | 1%  |

| $\tau$    | 0.0  | 0.1 | 0.2 | 0.3 | 0.4 | 0.5 |
|-----------|------|-----|-----|-----|-----|-----|
| Charge    | 0%   | 10% | 18% | 26% | 33% | 39% |
| Discharge | 100% | 90% | 82% | 74% | 67% | 61% |
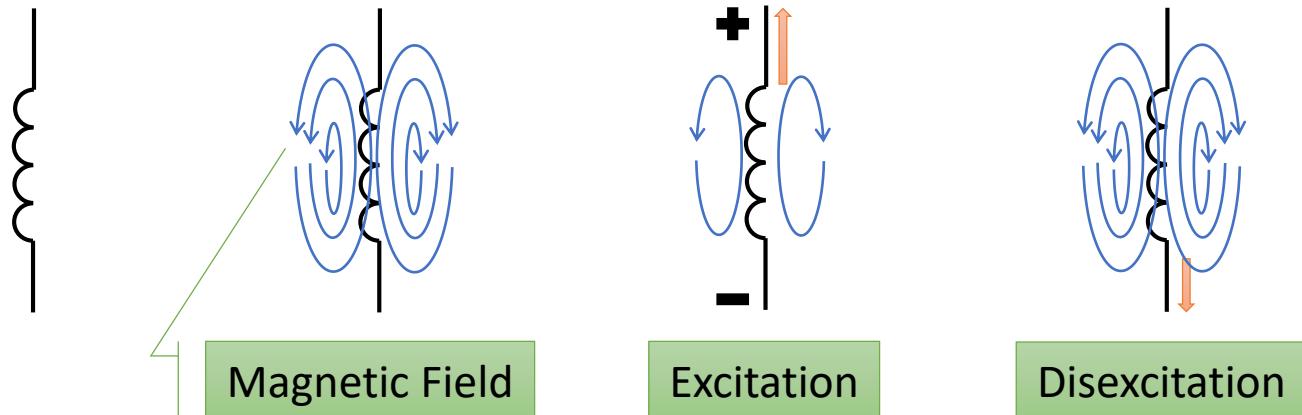
# Inductors (1)

- Basic Features
  - Stores electric energy when current flows through it
  - The energy gets stored in a magnetic field
  - A magnetic field can be excited and disexcited
  - The induced current opposes the change of the field



# Inductors (2)

- Excitation
  - Basic Relations

$$\bullet R = \frac{U}{I}$$

$$\bullet U_L = -L \frac{dI}{dt} = -LI\dot{}$$


- Kirchhoff's circuit law

$$\bullet U_R - U_L - U = 0$$

$$\bullet RI + LI\dot{} - U = 0$$



- Differential Equation
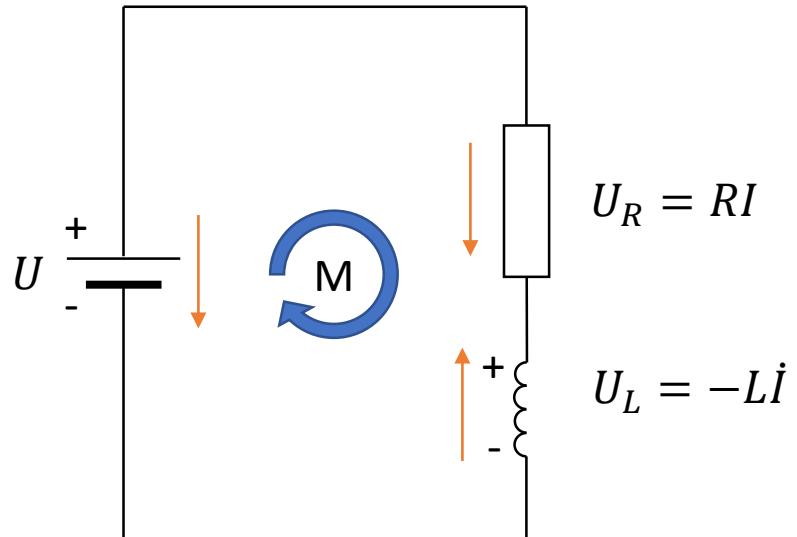
$$\bullet \dot{I} = \frac{1}{L}U - \frac{R}{L}I$$


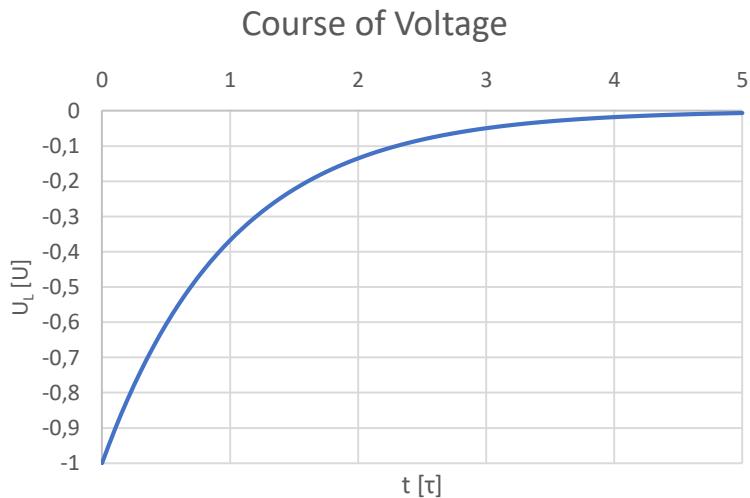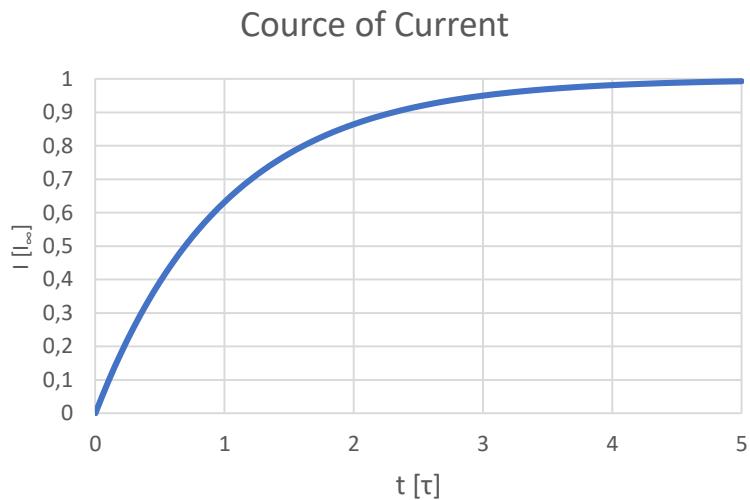
# Inductors (3)

- Excitation (continued)
  - Solution of the equation
    - $I = \frac{U}{R} \left(1 - e^{-\frac{R}{L}t}\right)$
    - $\tau = \frac{L}{R}$  (time constant)
  - Course of the current
    - $I = \frac{U}{R} \left(1 - e^{-\frac{t}{\tau}}\right)$
  - Course of the voltage
    - $U_L = -LI$
    - $U_L = -Ue^{-\frac{t}{\tau}}$



# Inductors (4)

- Disexcitation
  - Basic Relations

$$\bullet R = \frac{U}{I}$$

$$\bullet U_L = -L \frac{dI}{dt} = -LI\dot{}$$


- Kirchhoff's circuit law

$$\bullet U_R + U_L = 0$$

$$\bullet RI - LI\dot{ } = 0$$

- Differential Equation

$$\bullet \dot{I} = \frac{R}{L} I$$

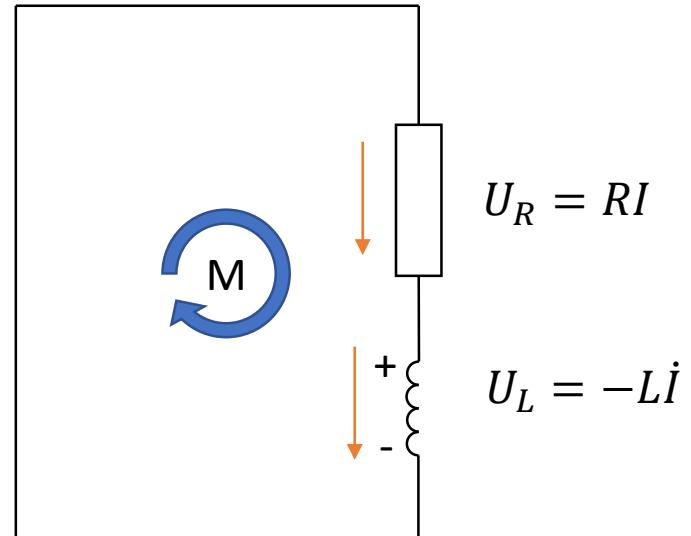

# Capacitors (5)

- Disexcitation (continued)
  - Solution of the equation
    - $I = \frac{U}{R} e^{-\frac{R}{L}t}$
    - $\tau = \frac{L}{R}$  (time constant)
  - Course of the current
    - $I = \frac{U}{R} e^{-\frac{t}{\tau}}$
  - Course of the voltage
    - $U_L = -LI$
    - $U_L = U e^{-\frac{t}{\tau}}$

