

Kinds of Circuits


Networks and Embedded Software

First Grade Level

by Wolfgang Neff


Combinational Circuits

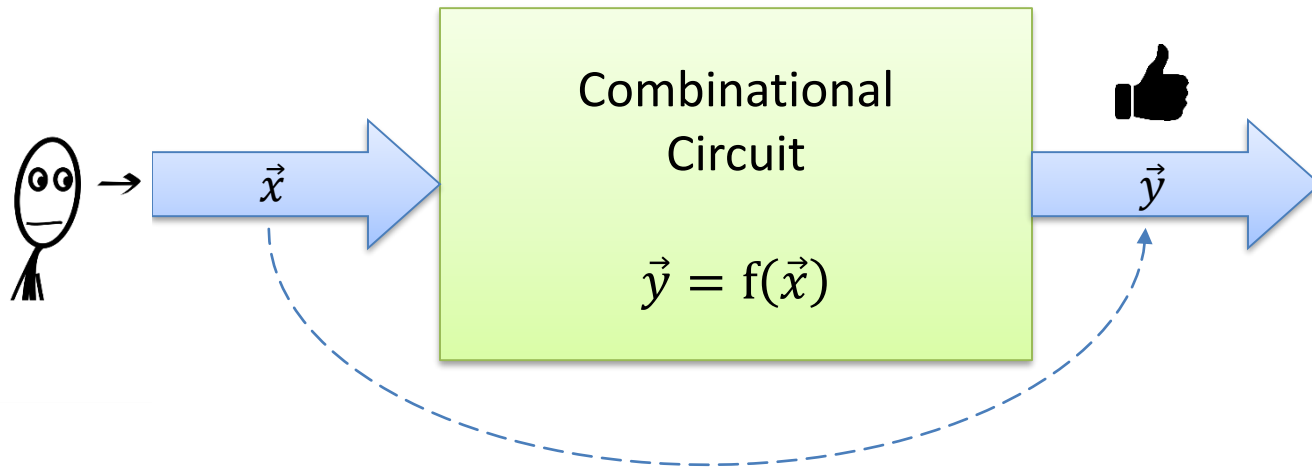- Output depends on current input, only
 - Output is a function of input
 - Time is of no importance
 - System does not remember




Sequential Circuits (1)

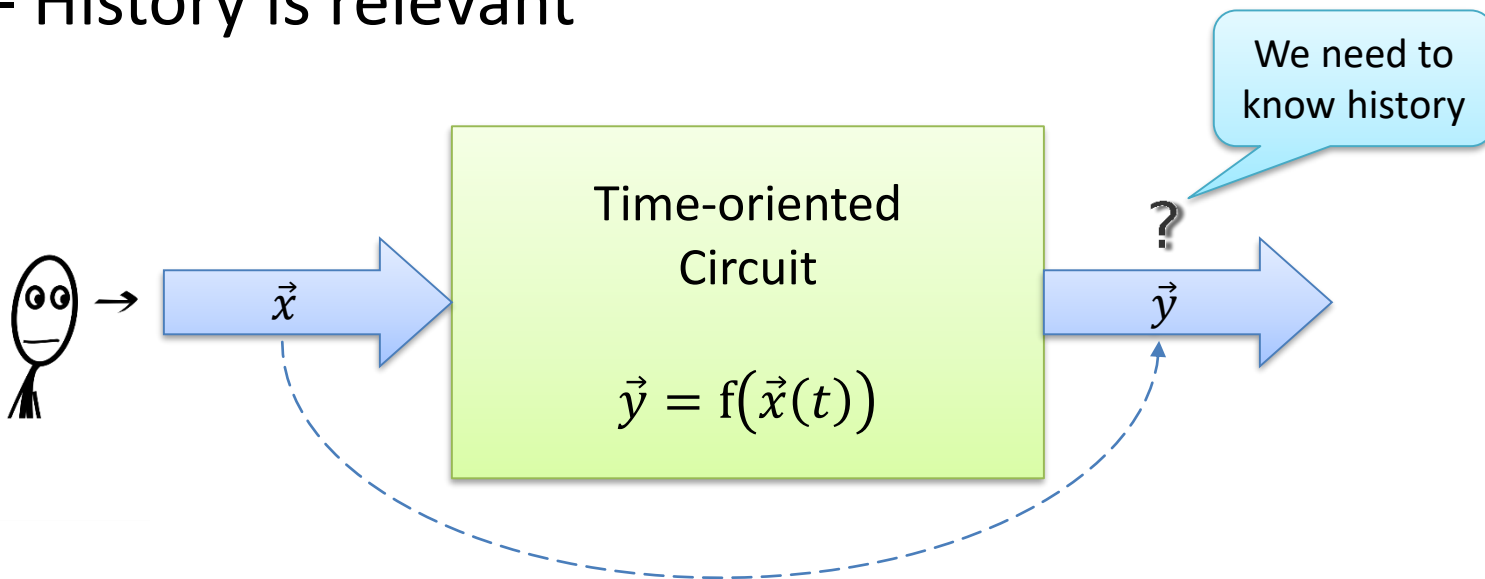- Output depends on previous inputs
 - Output is a function of input and time
 - History is relevant




Sequential Circuits (2)

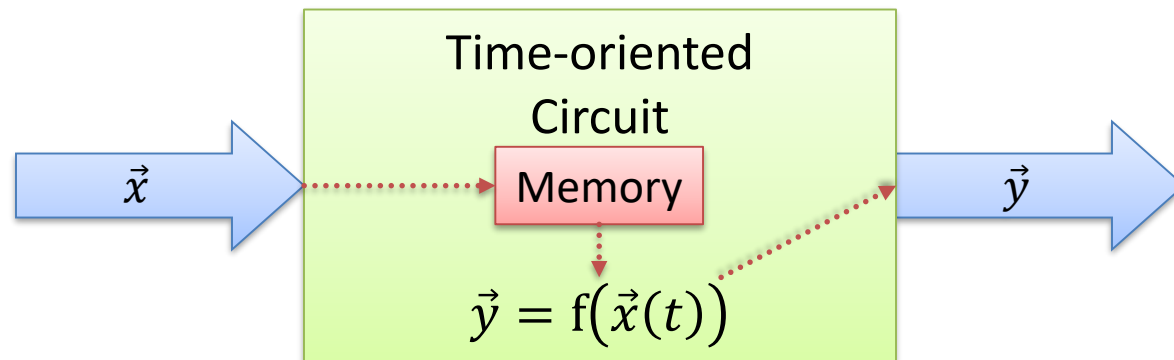- Output depends on previous inputs (continued)
 - A memory is required




Sequential Circuits (3)

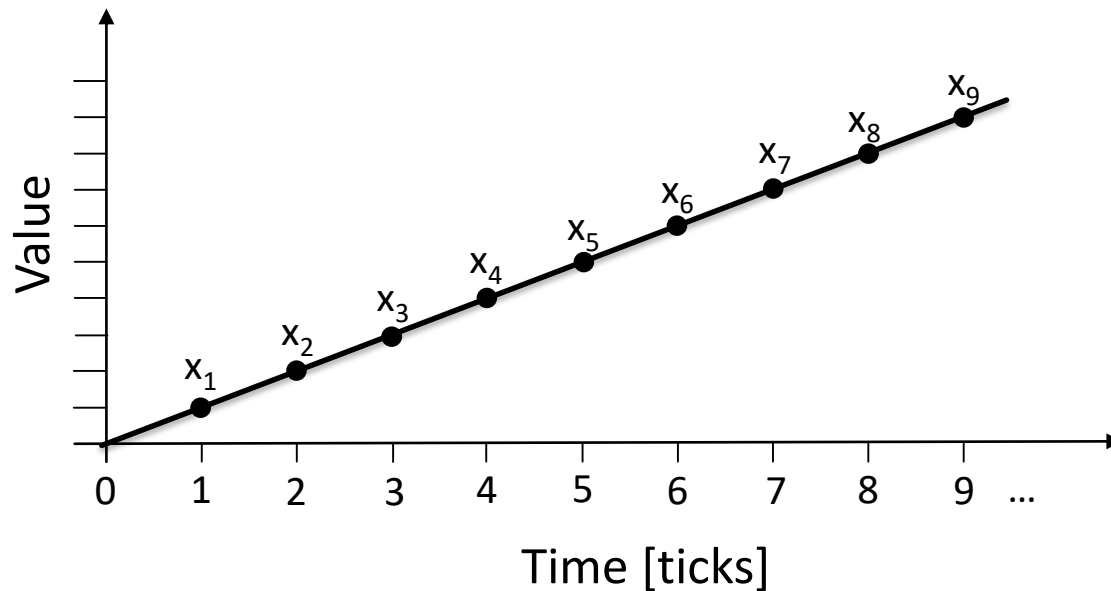- How to handle history
 - Time gets discretized
 - Time becomes a sequence




Sequential Circuits (4)

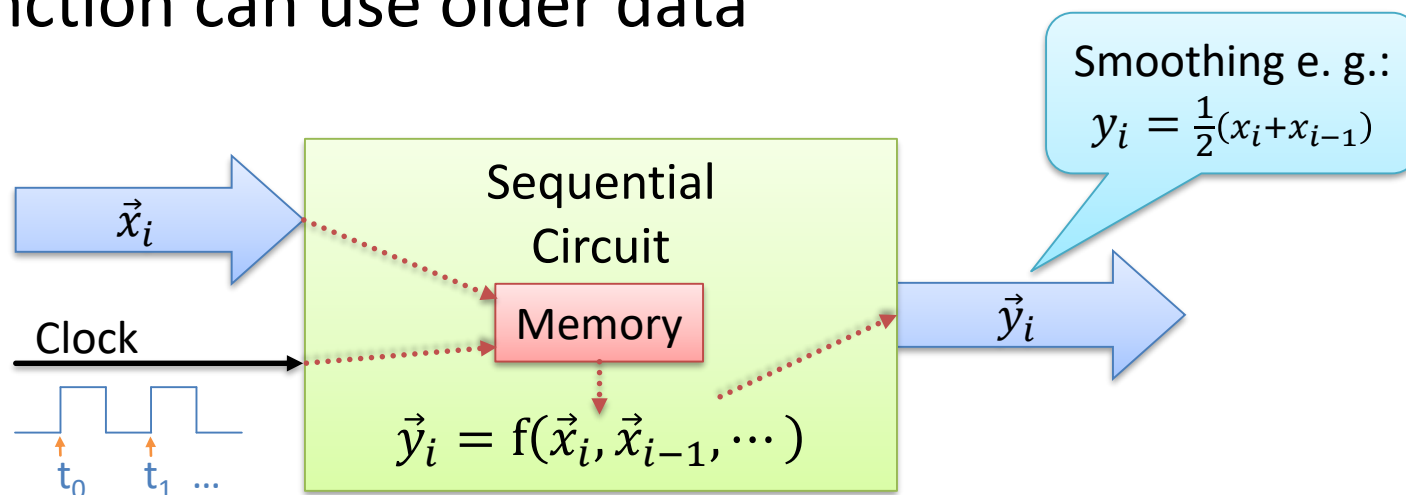- Time is provided by a clock
 - Input becomes a sequence of data
 - Function can use older data



Sequential Circuits (5)

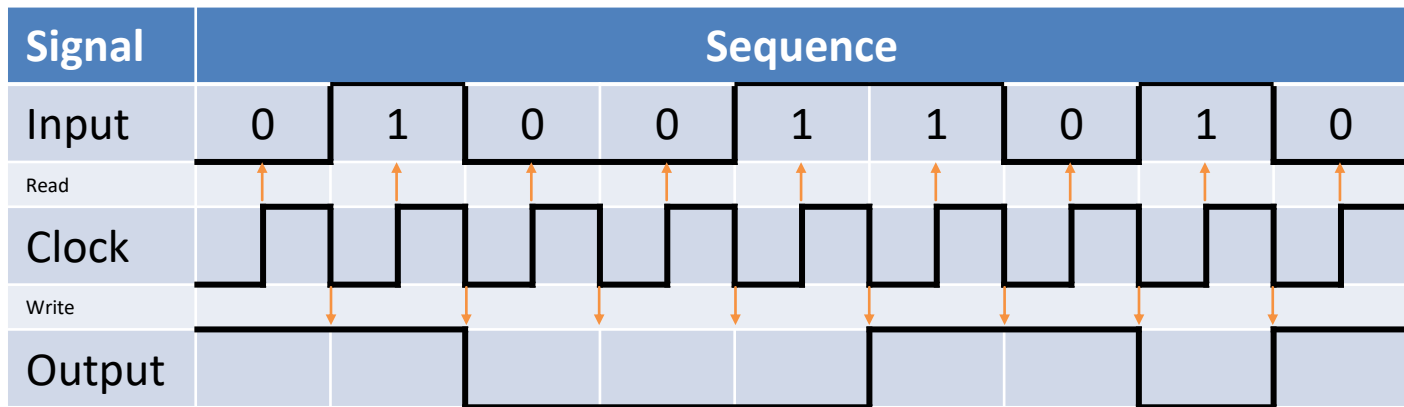- Taking processing time into account
 - Input and output are separated
 - Circuit reads input on rising edge
 - Circuit writes output on falling edge




Pulse Diagram

Sequential Circuits (6)

- Sequential circuits often just store states
 - States are handled by state machines (FSM)
 - They are represented by state diagrams
 - They have


- States
- Transitions
- Conditions

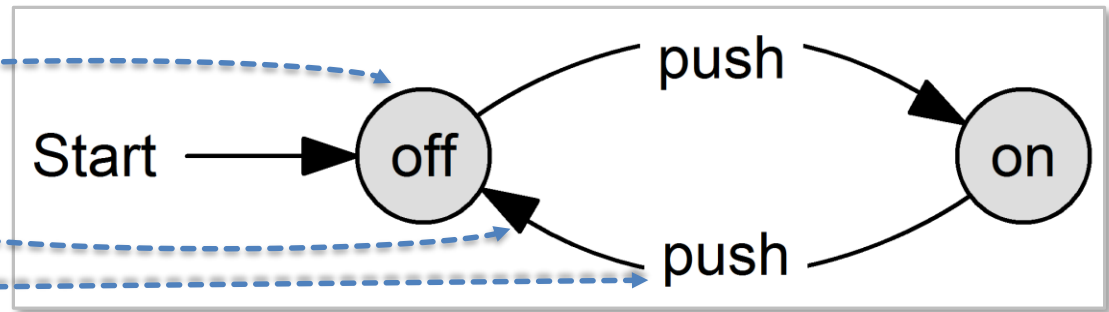

State Diagram of a Switch

Sequential Circuits (7)

- States are stored by D flip-flops

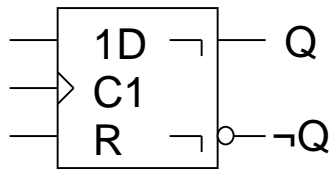

D	Q ⁺
0	0
1	1

- *1D*: Synchronous data line controlled by clock 1
- *C1*: First clock signal of the circuit
- *R*: Asynchronous reset line
- *Q*: Stored state