

Sequential Circuits


Mechanical and Electrical Engineering

Second Grade Level

by Wolfgang Neff

Sequential Circuits (1)

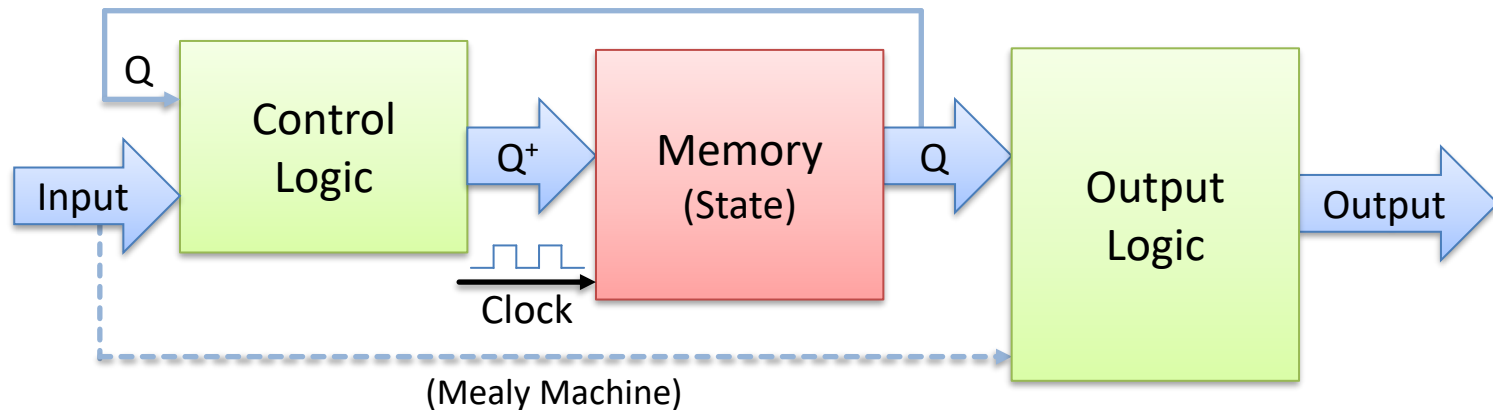- Two representations are frequently used
 - Mealy Machine (dashed arrow allowed)
 - Moore Machine (dashed arrow not allowed)



Sequential Circuits (2)

- Design process
 - Create state diagram
 - Number of states
 - Transitions and conditions
 - Encode states
 - One D flip-flops per bit
 - Design control logic
 - State/transition table
 - Design output logic


Sequential Circuits (3)

- Example I

- Assignment

Design a sequential circuit which outputs 1 if an even number of 1 was read.

- State diagram

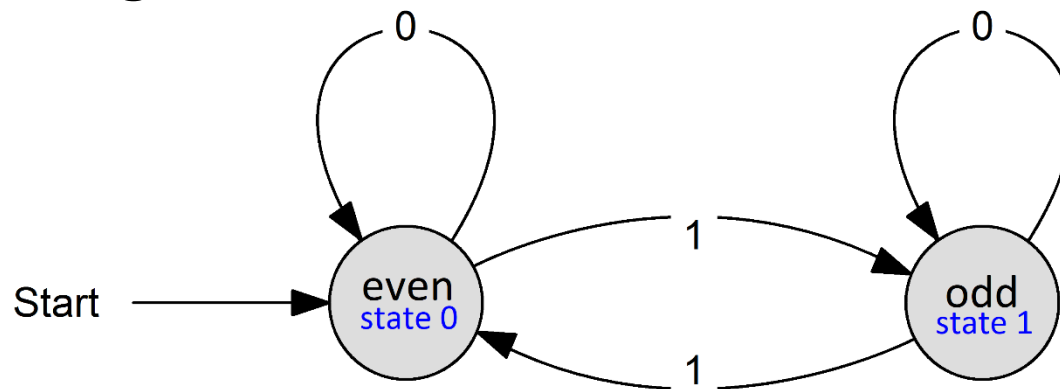

Sequential Circuits (4)

- Example I (continued)

- Number of states

- Even, odd \rightarrow 2 states \rightarrow 1 bit \rightarrow 1 D flip-flop

- State table (transitions and conditions)

Q	a	Q ⁺
Even (0)	0	Even (0)
Even (0)	1	Odd (1)
Odd (1)	0	Odd (1)
Odd (1)	1	Even (0)

a Input

Q Current State

Q^+ Next State

Sequential Circuits (5)

- Example I (continued)


- Encoding of states

- Even bit count: 0, 2, 4, 6, ...
 - Odd bit count: 1, 3, 5, 7, ...

State	Encoding
Even	0
Odd	1

- Output logic


Q	y
0	1
1	0

 $y(Q) = \neg Q$

Sequential Circuits (6)

- Example I (continued)
 - Control logic


Q	a	Q ⁺
0	0	0
0	1	1
1	0	1
1	1	0

 

$$Q^+ = Q \oplus a$$


Sequential Circuits (7)

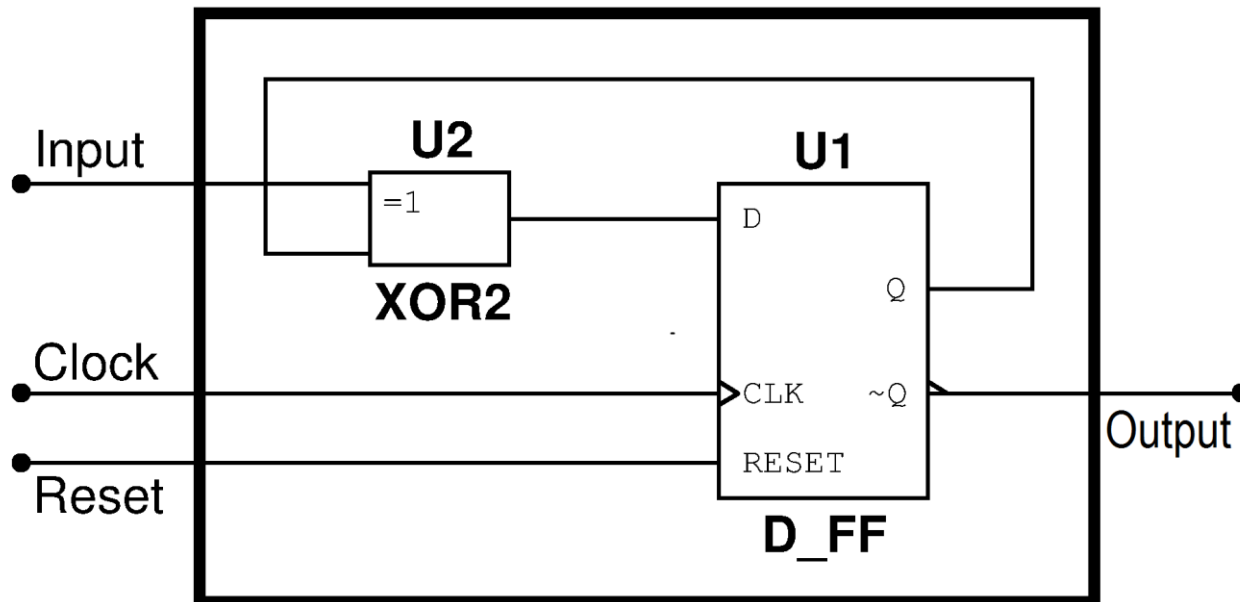- Example I (finished)
 - The resulting sequential circuit



Sequential Circuits (8)

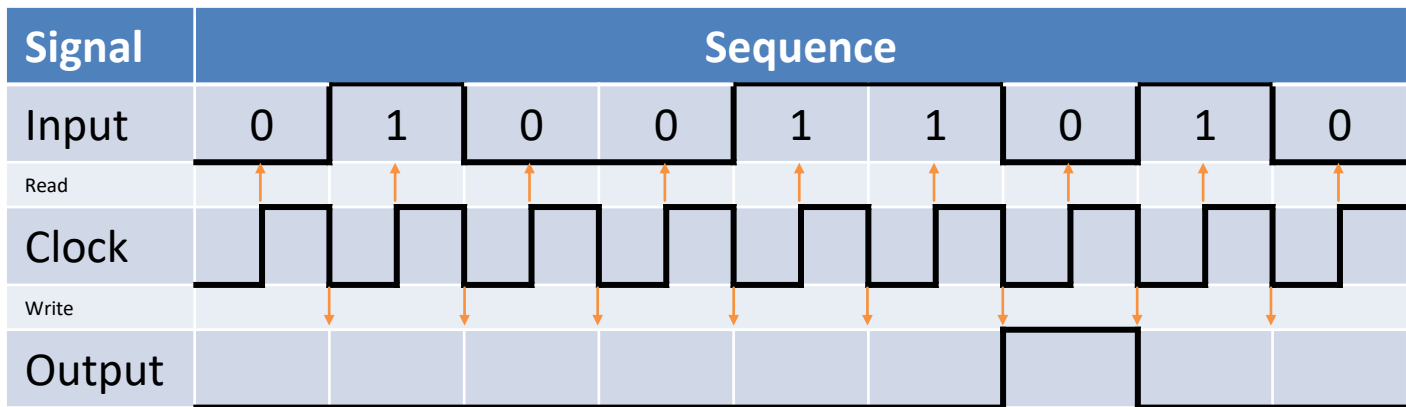
- Example II
 - Assignment
- Find two subsequent *1* in a bit sequence



Pulse Diagram

Sequential Circuits (9)

 - Example II (continued)
 - Number of states
 - None, one, two ones \rightarrow 3 states \rightarrow 2 bits
 - State diagram



Sequential Circuits (10)

- Example II (continued)
 - Control logic

Q_1	Q_0	a	Q_1^+	Q_0^+
0	0	0	0	0
0	0	1	0	1
0	1	0	0	0
0	1	1	1	0
1	0	0	0	0
1	0	1	1	0
1	1	0	X	X
1	1	1	X	X



State	Encoding
None	$0 \rightarrow 00$
One	$1 \rightarrow 01$
Two	$2 \rightarrow 10$

$$Q_0^+ = a \wedge \neg Q_0 \wedge \neg Q_1$$

$$Q_1^+ = (a \wedge Q_1) \vee (a \wedge Q_0)$$

Sequential Circuits (11)

- Example II (finished)

– Output logic

Q_1	Q_0	y
0	0	0
0	1	0
1	0	1
1	1	X

$$y = Q_1$$

